

- CSE 331 -
Computer Organization

HW3 Report

(Esra Eryılmaz 171044046)

Unsigned Number Multiplier using Logisim :

My design has 3 parts:


- Datapath (contains required operations : add, shift etc..)
- Control Unit (implements ASM)
- Mult32 (main)

Also I designed, (inside datapath) (bonus)

- 32 bit adder
- 64 bit shifter (1-bit logical right shifter)

➤ Control Unit Design

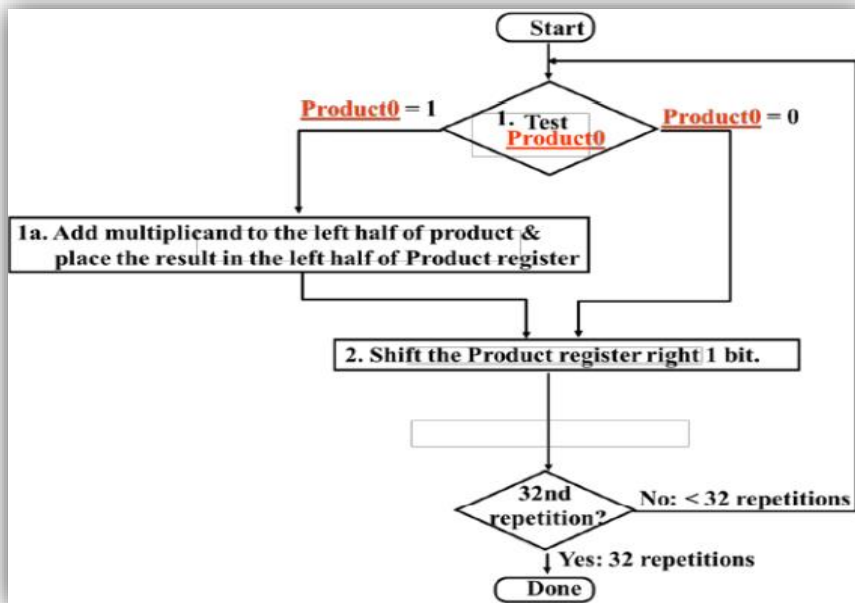Control Unit will implement the given ASM:



Updated ASM →

States:

S0, S1, S2,
S3, S4, S5


Input signals:

Start, P0eq,
P0lt, Ceq, Clt

Output signals:

(input for datapath)

La, Lp, Lc,
Sump, Shp, Lr

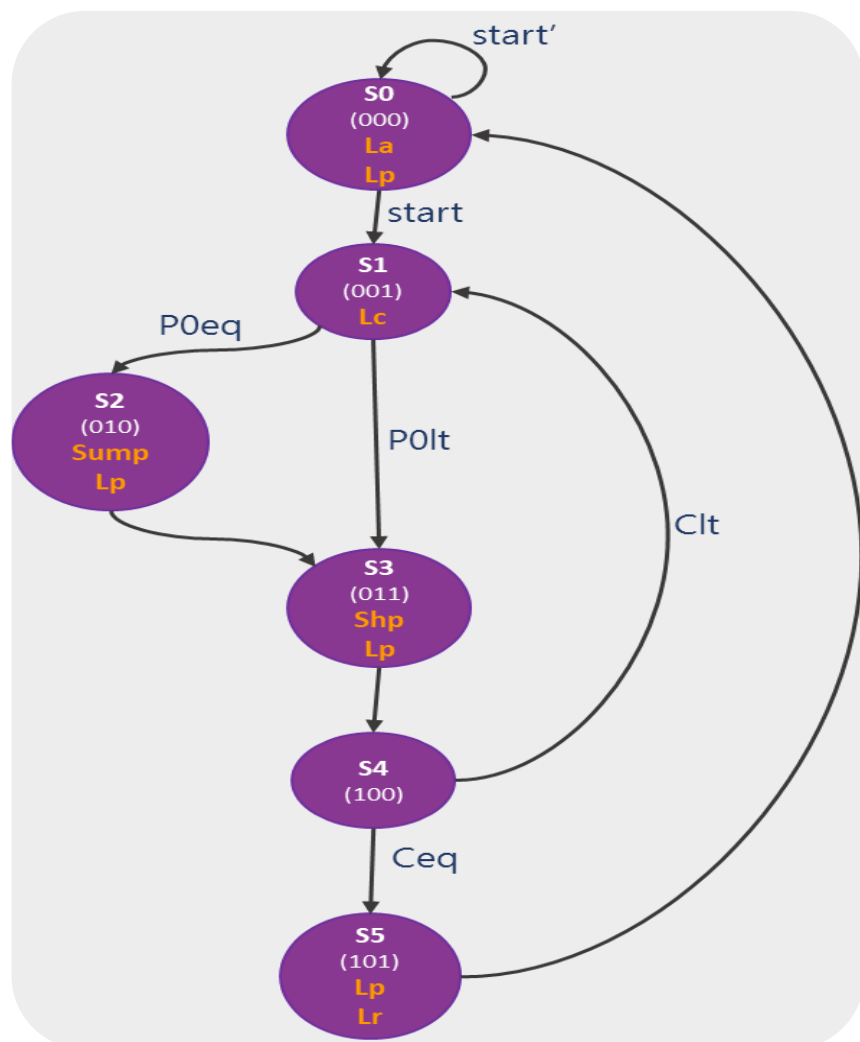

Truth Tables:

| Present States (PS) | | | Inputs | | | | | | Next States (NS) | | |
|---------------------|----|----|--------|-------|------|------|-----|-----|------------------|----|----|
| | P2 | P1 | P0 | start | P0eq | P0lt | Ceq | Clf | N2 | N1 | N0 |
| S0 | 0 | 0 | 0 | 0 | - | - | - | - | 0 | 0 | 0 |
| | 0 | 0 | 0 | 1 | - | - | - | - | 0 | 0 | 1 |
| S1 | 0 | 0 | 1 | - | 1 | 0 | - | - | 0 | 1 | 0 |
| | 0 | 0 | 1 | - | 0 | 1 | - | - | 0 | 1 | 1 |
| S2 | 0 | 1 | 0 | - | - | - | - | - | 0 | 1 | 1 |
| S3 | 0 | 1 | 1 | - | - | - | - | - | 1 | 0 | 0 |
| S4 | 1 | 0 | 0 | - | - | - | 0 | 1 | 0 | 0 | 1 |
| | 1 | 0 | 0 | - | - | - | 1 | 0 | 1 | 0 | 1 |
| S5 | 1 | 0 | 1 | - | - | - | - | - | 0 | 0 | 0 |

Outputs are just depends on states, so I showed it in separate truth table:

| Present States (PS) | | | | | | | | | |
|---------------------|----|----|----|----|----|----|------|-----|----|
| | P2 | P1 | P0 | La | Lp | Lc | Sump | Shp | Lr |
| S0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| S1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| S2 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| S3 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| S4 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| S5 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |

Boolean expressions from truth table:

$$N2 = P2'P1P0 + P2P1'P0'Ceq$$

$$N1 = P2'P1'P0P0eq + P2'P1'P0P0lt + P2'P1P0'$$

$$N0 = P2'P1'P0'start + P2'P1'P0P0lt + P2'P1P0' + P2P1'P0'Clf + P2P1'P0'Ceq$$

$$La = S0$$

$$Lp = S0 + S2 + S3 + S5$$

$$Lc = S1$$


$$Sump = S2$$

$$Shp = S3$$

$$Lr = S5$$


➤ Mult32

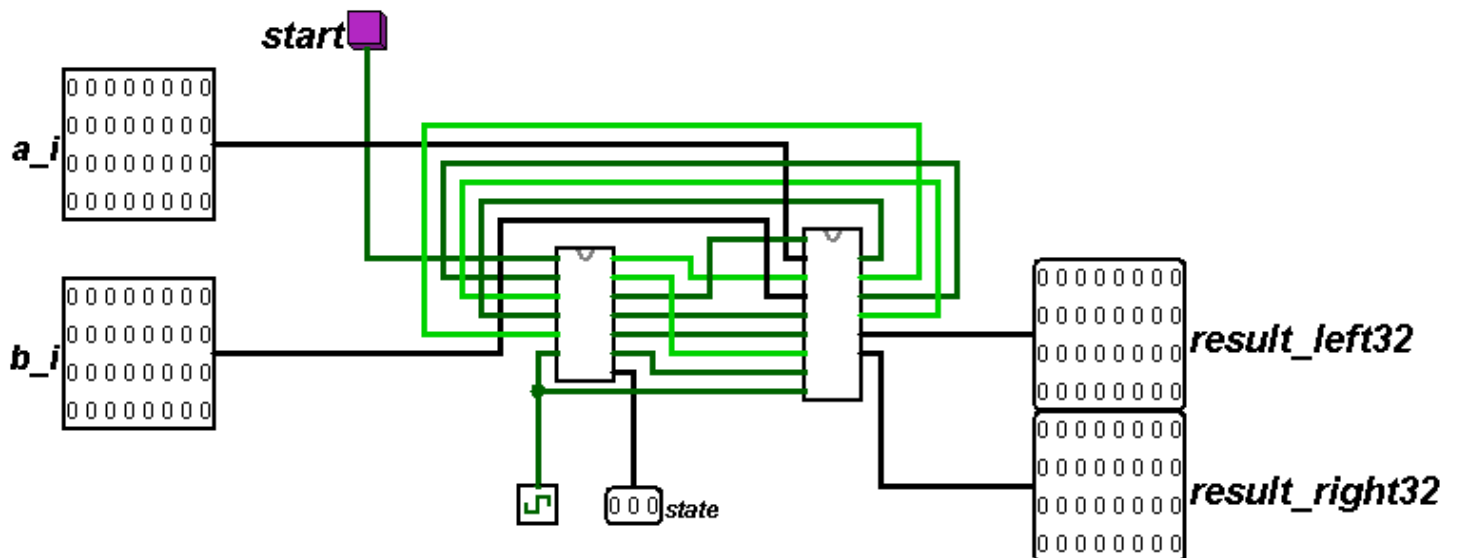Mult32: main file which combines datapath and control unit.




➤ Test Cases


- **Test1** → $3 \times 5 = 15$

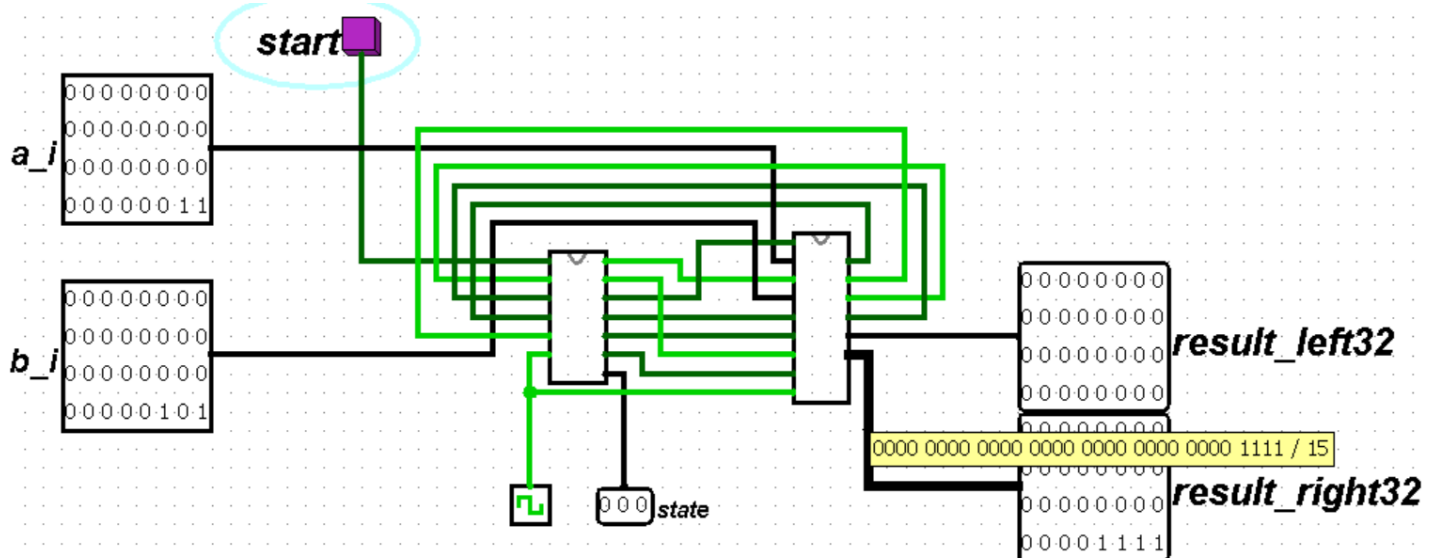


• **Test2** → $10 \times 33 = 330$

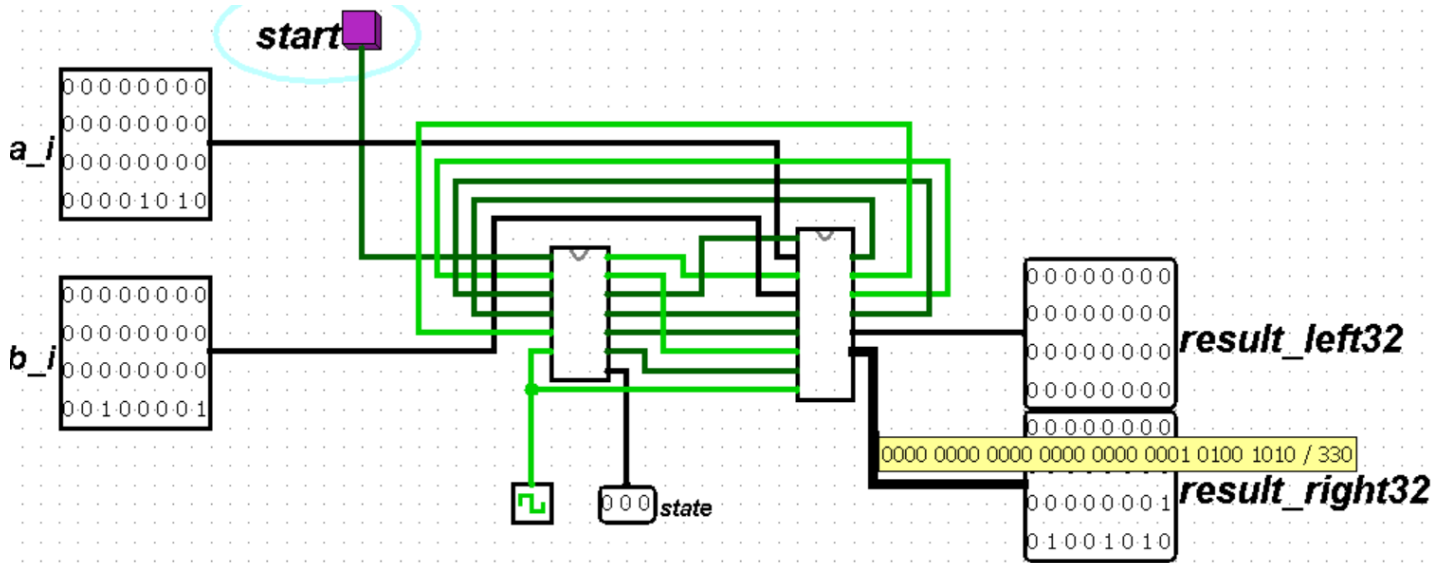


• **Test3** → $15 \times 15 = 225$

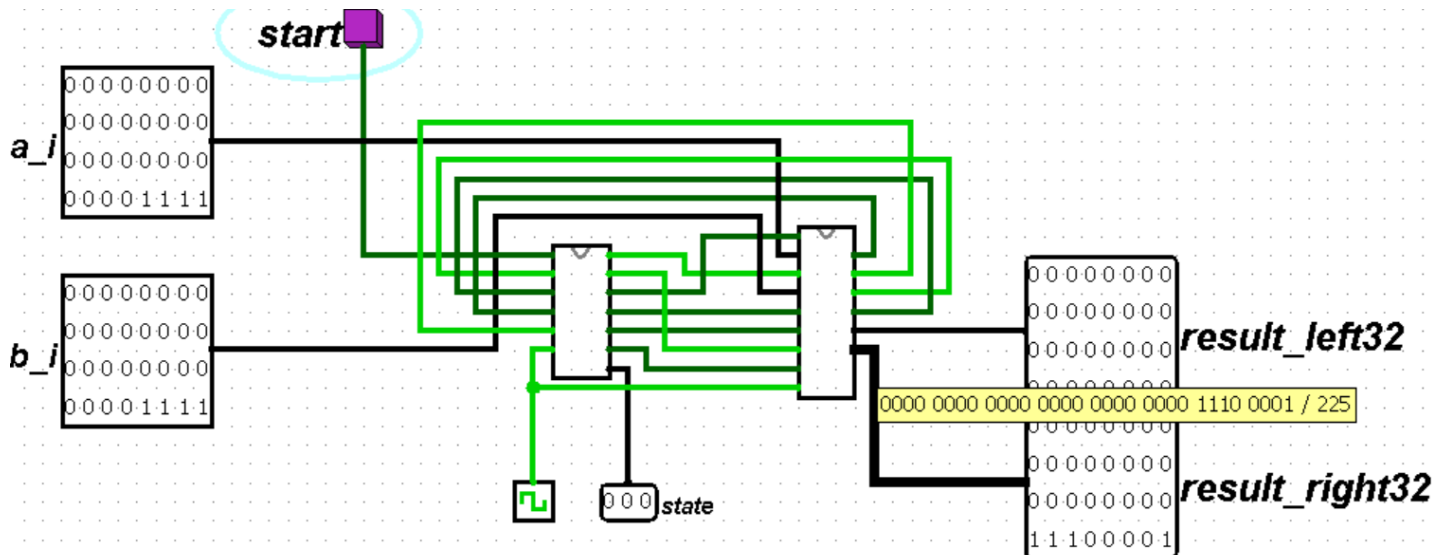

• **Test4** → $100 \times 101 = 10100$

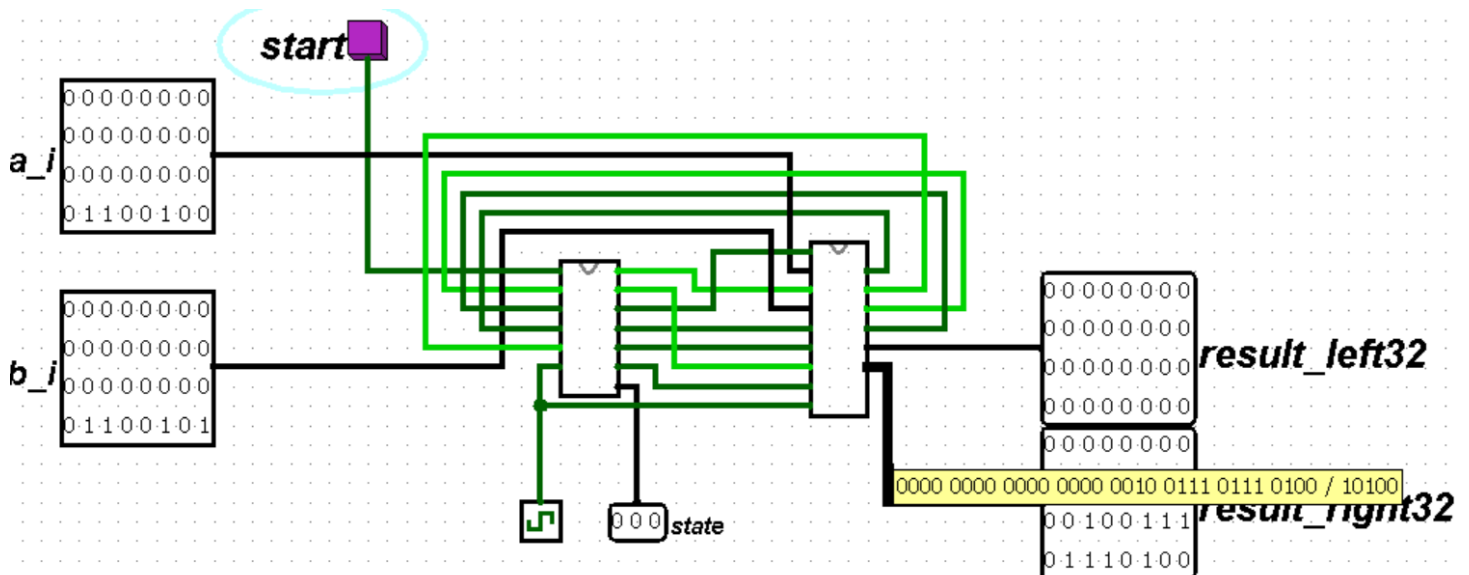

• **Test5** → $25 \times 12 = 300$

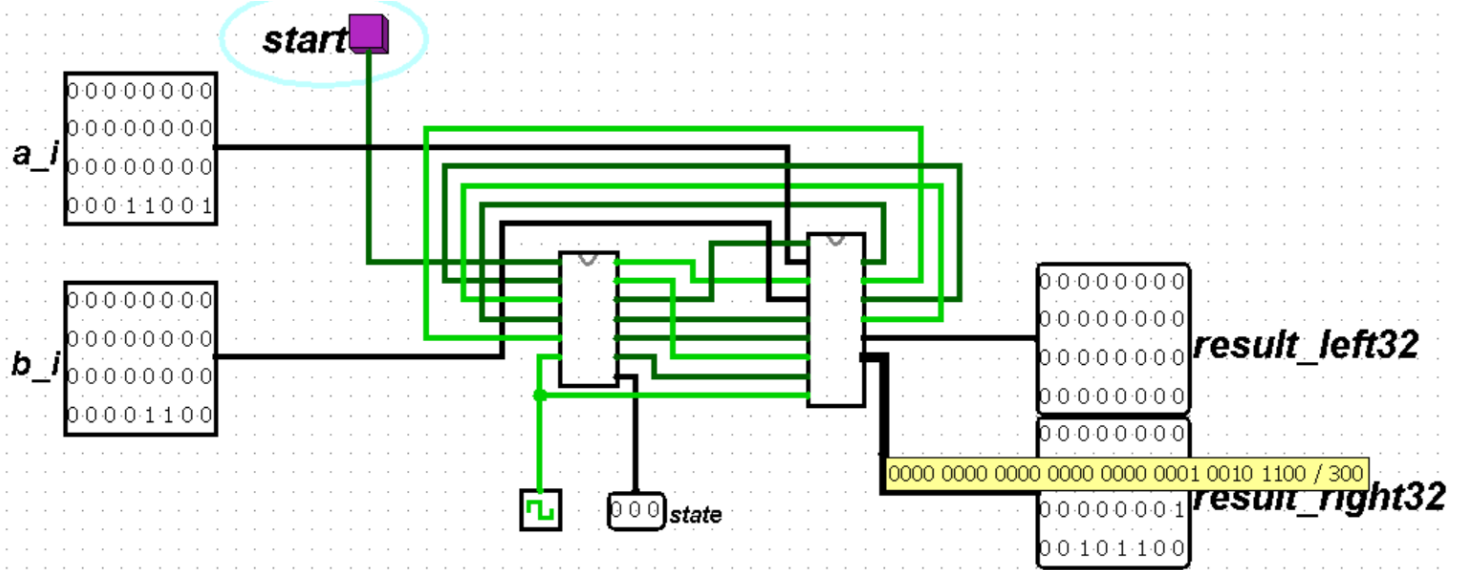

• **Test6** → $1500 \times 1450 = 2175000$

